
Lecture4(part1)


Topics covered:
Arithmetic



Number representation

Integers are represented as binary vectors

 Suppose each word consists of 32 bits, labeled 0...31.



MSB (most significant bit)

LSB (least)

Value of the binary vector interpreted as unsigned integer is:

$$V(b) = b_{31} \cdot 2^{31} + b_{30} \cdot 2^{30} + b_{29} \cdot 2^{29} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0$$

More generally in N bits,

$$V(b) = \sum_{n=0}^{n=N-1} b_n 2^n$$



Number representation (contd..)

- ❑ We need to represent both positive and negative integers.
- ❑ Three schemes are available for representing both positive and negative integers:
 - ◆ Sign and magnitude.
 - ◆ 1's complement.
 - ◆ 2's complement.
- ❑ All schemes use the Most Significant Bit (MSB) to carry the sign information:
 - ◆ If $MSB = 0$, bit vector represents a positive integer.
 - ◆ If $MSB = 1$, bit vector represents a negative integer.



Number representation (contd..)

□ Sign and Magnitude:

- ◆ Lower $N-1$ bits represent the magnitude of the integer
- ◆ MSB is set to 0 or 1 to indicate positive or negative

□ 1's complement:

- ◆ Construct the corresponding positive integer (MSB = 0)
- ◆ Bitwise complement this integer

□ 2's complement:

- ◆ Construct the 1's complement negative integer
- ◆ Add 1 to this



Number representation (contd..)

B $b_3 b_2 b_1 b_0$	Values represented		
	Sign and magnitude	1's complement	2's complement
0 1 1 1	+ 7	+ 7	+ 7
0 1 1 0	+ 6	+ 6	+ 6
0 1 0 1	+ 5	+ 5	+ 5
0 1 0 0	+ 4	+ 4	+ 4
0 0 1 1	+ 3	+ 3	+ 3
0 0 1 0	+ 2	+ 2	+ 2
0 0 0 1	+ 1	+ 1	+ 1
0 0 0 0	+ 0	+ 0	+ 0
1 0 0 0	- 0	- 7	- 8
1 0 0 1	- 1	- 6	- 7
1 0 1 0	- 2	- 5	- 6
1 0 1 1	- 3	- 4	- 5
1 1 0 0	- 4	- 3	- 4
1 1 0 1	- 5	- 2	- 3
1 1 1 0	- 6	- 1	- 2
1 1 1 1	- 7	- 0	- 1



Number representation (contd..)

Range of numbers that can be represented in N bits

Unsigned: $0 < V(b) < 2^N - 1$

Sign and magnitude: $-2^{N-1} - 1 < V(b) < 2^{N-1} - 1$
0 has both positive and negative representation

One's complement:: $-2^{N-1} - 1 < V(b) < 2^{N-1} - 1$
0 has both positive and negative representation

Two's complement:: $-2^{N-1} < V(b) < 2^{N-1} - 1$
0 has a single representation, easier to add/subtract.



Value of a bit string in 2's complement

How to determine the value of an integer given:

Integer occupies N bits.

2's complement system is in effect.

Binary vector b represents a negative integer, what is $V(b)$.

Write

$$b = \mathbf{1} b_{n-1} b_{n-2} b_{n-3} \dots b_1 b_0$$

Then

$$V(b) = -2^{n-1} + b_{n-2}2^{n-2} + b_{n-3}2^{n-3} + \dots + b_22^2 + b_12^1 + b_02^0$$

$$(v(b) = \mathbf{-2^{n-1}} + b_{n-2}2^{n-2} + b_{n-3}2^{n-3} + \dots + b_22^2 + b_12^1 + b_02^0$$

*showing **negative** and **positive** parts of the expression)*

So, in 4 bits, 1011 is

$$v(1011) = -8 + 3 = -5$$



Addition of positive numbers

Add two one-bit numbers

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

↑
Carry-out

To add multiple bit numbers:

- Add bit pairs starting from the low-order or LSB (right end of bit vector)
- Propagate carries towards the high-order or MSB (left end of bit vector)



Addition and subtraction of signed numbers

- ❑ We need to add and subtract both positive and negative numbers.
- ❑ Recall the three schemes of number representation.
- ❑ Sign-and-magnitude scheme is the simplest representation, but it is the most awkward (inapplicable) for addition and subtraction operations. (has two forms for the zero number)
- ❑ 2's complement is the most efficient method for performing addition and subtraction of signed numbers.



Rules for addition and subtraction of signed numbers in 2's complement form

□ To add two numbers:

- ◆ Add their n -bit representations.
- ◆ Ignore the carry out from MSB position.
- ◆ Sum is the algebraically correct value in the 2's complement representation as long as the answer is in the range -2^{n-1} through $+2^{n-1} - 1$.

□ To subtract two numbers X and Y ($X-Y$):

- ◆ Form the 2's complement of Y .
- ◆ Add it to X using Rule 1.
- ◆ Result is correct as long as the answer lies in the range -2^{n-1} through $+2^{n-1} - 1$.



Addition Operations using Two's complement

The main advantage of using two's complement is converting subtraction into addition

$$\begin{array}{rcl} \text{(a)} & 0010 & (+2) \\ & + 0011 & (+3) \\ \hline & 0101 & (+5) \end{array}$$
$$\begin{array}{rcl} \text{(c)} & 1011 & (-5) \\ & + 1110 & (-2) \\ \hline & 1001 & (-7) \end{array}$$

$$\begin{array}{rcl} \text{(b)} & 0100 & (+4) \\ & + 1010 & (-6) \\ \hline & 1110 & (-2) \end{array}$$
$$\begin{array}{rcl} \text{(d)} & 0111 & (+7) \\ & + 1101 & (-3) \\ \hline & 0100 & (+4) \end{array}$$

Note: Don't forget to neglect the carry bit



Subtraction Operations using Two's complement

(e)	$\begin{array}{r} 1101 \\ - 1001 \\ \hline \end{array}$	$\begin{array}{r} (-3) \\ (-7) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 1101 \\ + 0111 \\ \hline 0100 \end{array}$	$\begin{array}{r} (+4) \\ \hline \end{array}$
(f)	$\begin{array}{r} 0010 \\ - 0100 \\ \hline \end{array}$	$\begin{array}{r} (+2) \\ (+4) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 0010 \\ + 1100 \\ \hline 1110 \end{array}$	$\begin{array}{r} (-2) \\ \hline \end{array}$
(g)	$\begin{array}{r} 0110 \\ - 0011 \\ \hline \end{array}$	$\begin{array}{r} (+6) \\ (+3) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 0110 \\ + 1101 \\ \hline 0011 \end{array}$	$\begin{array}{r} (+3) \\ \hline \end{array}$
(h)	$\begin{array}{r} 1001 \\ - 1011 \\ \hline \end{array}$	$\begin{array}{r} (-7) \\ (-5) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 1001 \\ + 0101 \\ \hline 1110 \end{array}$	$\begin{array}{r} (-2) \\ \hline \end{array}$
(i)	$\begin{array}{r} 1001 \\ - 0001 \\ \hline \end{array}$	$\begin{array}{r} (-7) \\ (+1) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 1001 \\ + 1111 \\ \hline 1000 \end{array}$	$\begin{array}{r} (-8) \\ \hline \end{array}$
(j)	$\begin{array}{r} 0010 \\ - 1101 \\ \hline \end{array}$	$\begin{array}{r} (+2) \\ (-3) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 0010 \\ + 0011 \\ \hline 0101 \end{array}$	$\begin{array}{r} (+5) \\ \hline \end{array}$

◆ Overflow in integer arithmetic

- ❑ When the result of an arithmetic operation is outside the representable range an arithmetic overflow has occurred.
 - ◆ Range is -2^{n-1} through $+2^{n-1} - 1$ for n-bit vector.
- ❑ When adding **unsigned** numbers, **carry-out** from the MSB position serves as the **overflow indicator**.
- ❑ When adding **signed** numbers, this does not work.
- ❑ Using 4-bit signed numbers, add +7 and +4:
 - ◆ Result is 1011, which represents -5.
- ❑ Using 4-bit signed integers, add -4 and -6:
 - ◆ Result is 0110, which represents +6.

0111(+7)
+ 0100(+4)

1011(-5) Overflow

1100(-4)
+ 1010(-6)

0110(+6) Overflow



Overflow in integer arithmetic (contd..)

- ❑ **Overflow** occurs when both the numbers have the same sign.
 - ◆ Addition of numbers with different signs cannot cause an overflow.
- ❑ Carry-out signal from the MSB (sign-bit) position is not a sufficient indicator of overflow when adding signed numbers.
- ❑ **Detect overflow** when adding X and Y :
 - ◆ Examine the signs of X and Y .
 - ◆ Examine the signs of the result S .
 - ◆ When X and Y have the same sign, and the sign of the result differs from the signs of X and Y , overflow has occurred.
 - ◆ How to detect overflow by a logical circuit?

Overflow = ??????????




Addition/subtraction of signed numbers

x_i	y_i	Carry-in c_i	Sum s_i	Carry-out c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

Example:

 

At the i^{th} stage:

Input:


c_i is the carry-in

Output:

s_i is the sum

c_{i+1} carry-out to $(i+1)^{st}$ state


◆ Addition logic for a single stage

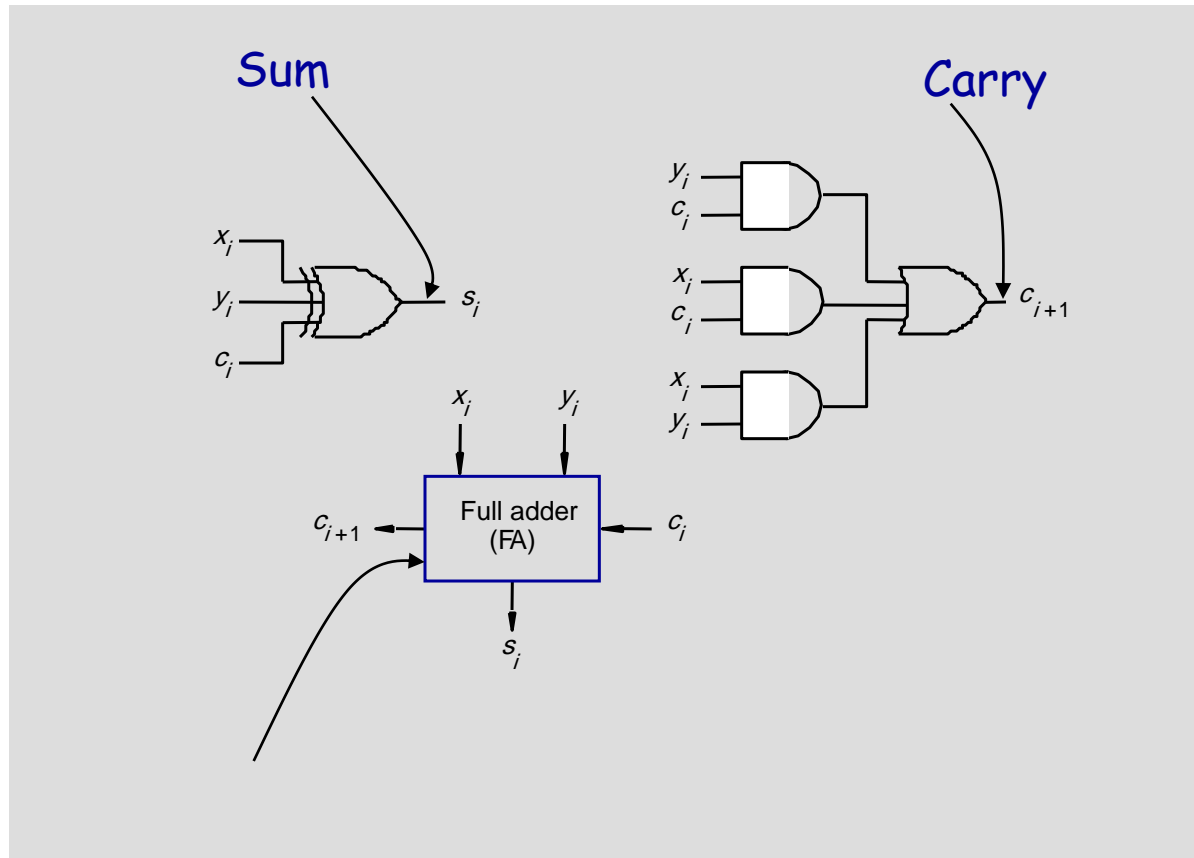


Full Adder (FA): Symbol for the complete circuit for a single stage of addition.

◆ n -bit subtractor

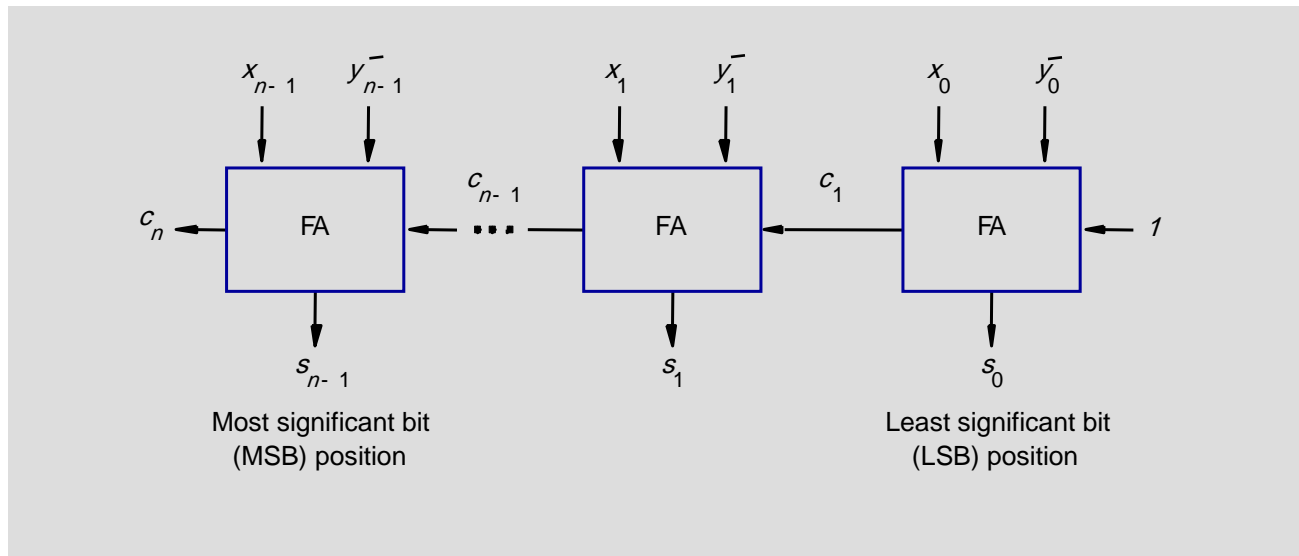
- Recall $X - Y$ is equivalent to adding 2's complement of Y to X .
- 2's complement is equivalent to 1's complement + 1.
- $X - Y = X + \bar{Y} + 1$
- 2's complement of positive and negative numbers is computed similarly.



n -bit adder/subtractor

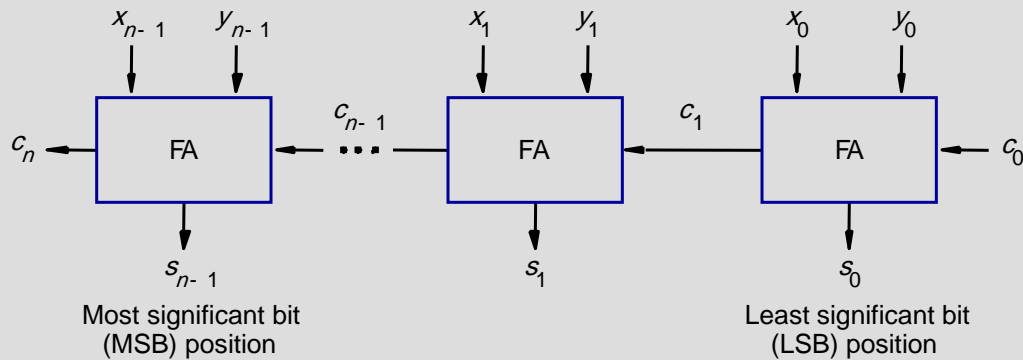


Adder inputs:
 $x_i, y_i, c_0=0$

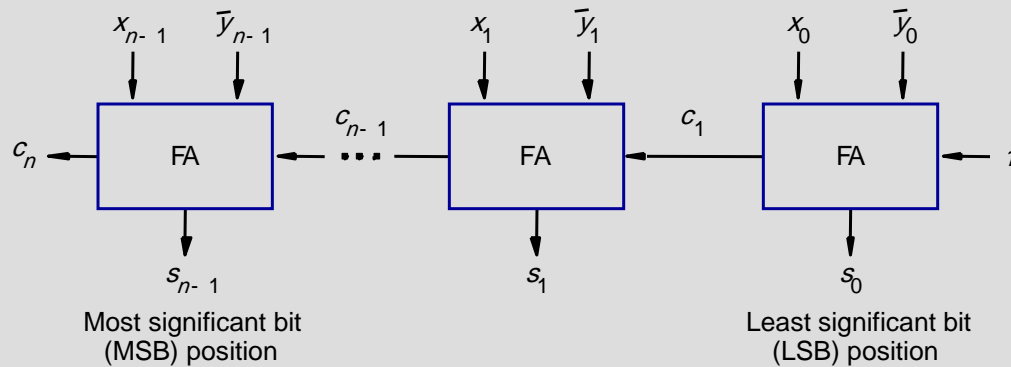

Subtractor inputs:
 $x_i, \bar{y}_i, c_0=1$



n -bit adder/subtractor (contd..)

 

- Add/sub control = 0, addition.
- Add/sub control = 1, subtraction.



Detecting overflows


- ❑ **Overflows** can only occur when the **sign** of the **two** operands is the **same**.
- ❑ **Overflow** occurs if the **sign** of the **result** is **different** from the **sign** of the **operands**.
- ❑ Recall that the MSB represents the sign.
 - ◆ x_{n-1} , y_{n-1} , s_{n-1} represent the sign of operand x , operand y and result s respectively.
- ❑ **Circuit** to **detect overflow** can be implemented by the following logic expressions:

$$\text{Overflow} = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$

$$\text{Overflow} = c_n \oplus c_{n-1}$$

◆ n -bit adder

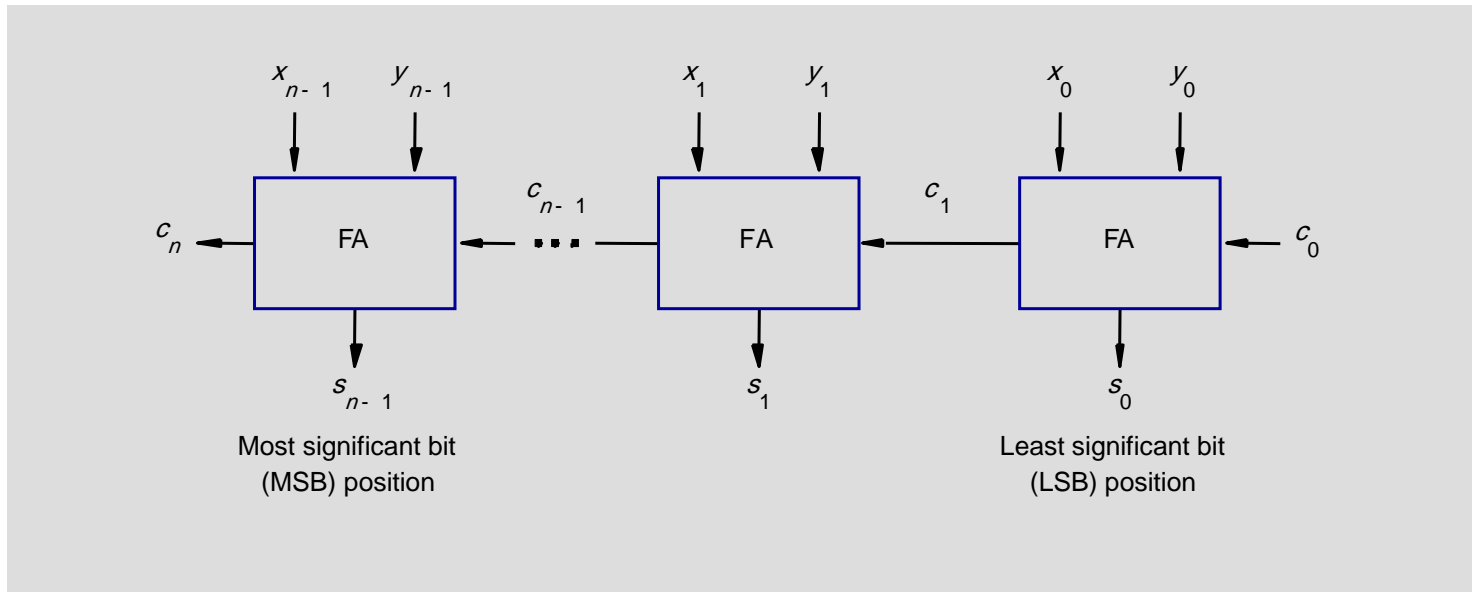
- Cascade n full adder (FA) blocks to form a n -bit adder.
- Carries propagate or ripple through this cascade, n -bit ripple carry adder.



Carry-in c_0 into the LSB position provides a convenient way to perform subtraction.


◆ kn -bit adder

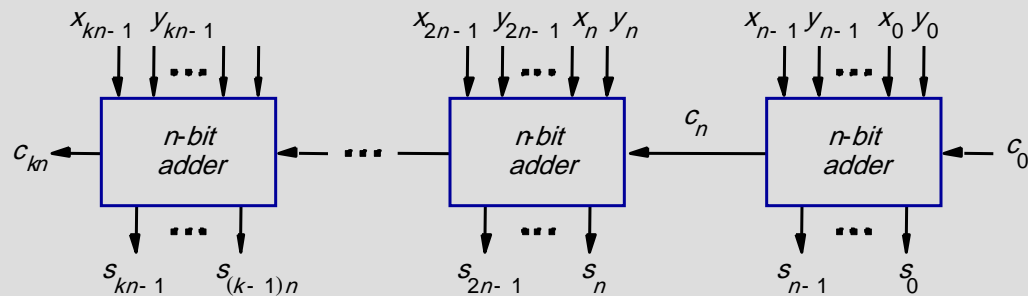K n -bit numbers can be added by cascading k n -bit adders.




Each n -bit adder forms a **block**, so this is cascading of blocks.
Carries ripple or propagate through blocks, Blocked Ripple Carry Adder

Computing the add time

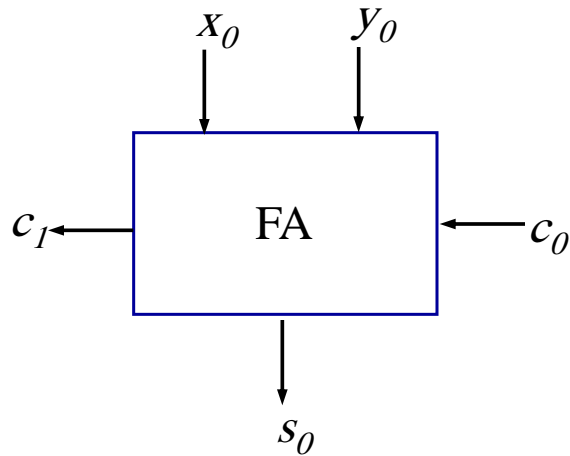


Consider 0^{th} stage:

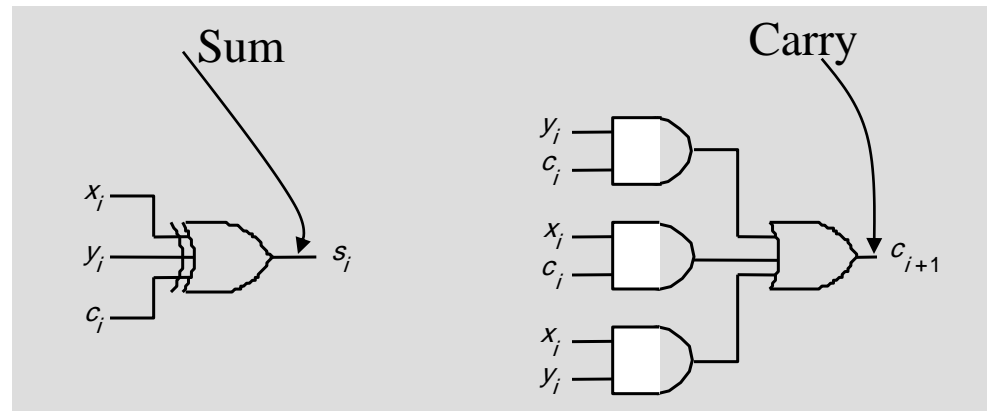- c_1 is available after 2 gate delays.
- s_1 is available after 1 gate delay.



◆ Computing the add time (contd..)

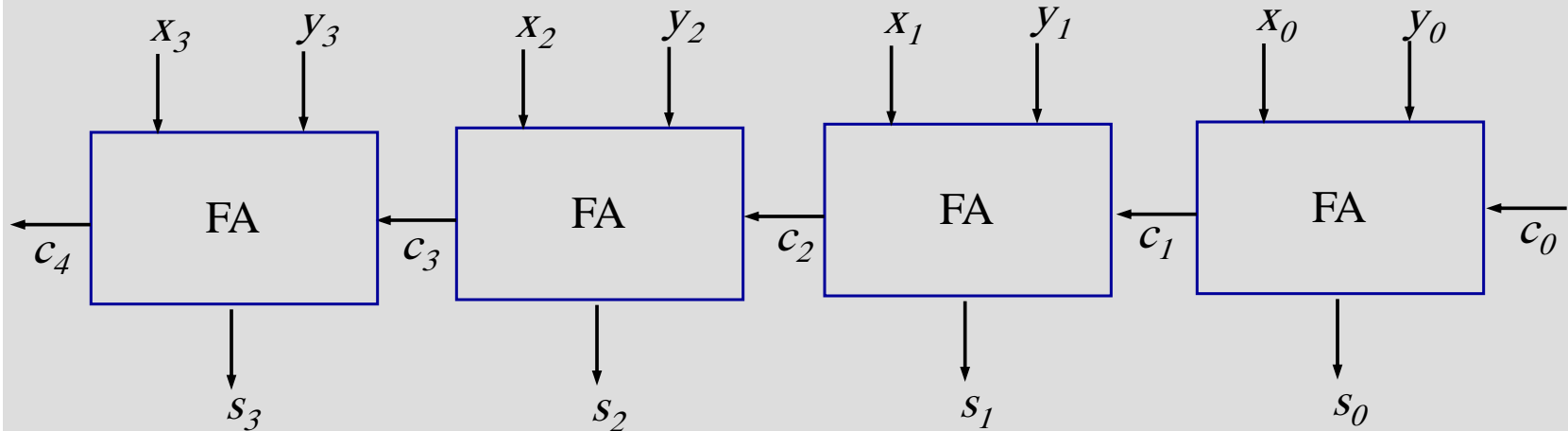Cascade of 4 Full Adders, or a 4-bit adder



- s_0 available after 1 gate delays, c_1 available after 2 gate delays.
- s_1 available after 3 gate delays, c_2 available after 4 gate delays.
- s_2 available after 5 gate delays, c_3 available after 6 gate delays.
- s_3 available after 7 gate delays, c_4 available after 8 gate delays.

For an n -bit adder, s_{n-1} is available after $2n-1$ gate delays
 c_n is available after $2n$ gate delays.



Fast addition

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- G_i is called generate function and P_i is called propagate function
- G_i and P_i are computed only from x_i and y_i and not c_i , thus they can be computed in one gate delay after X and Y are applied to the inputs of an n -bit adder.



Carry lookahead

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing


$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$

until


$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- All **carries** can be obtained **3 gate delays** after X , Y and c_0 are applied.
 - **One** gate delay for P_i and G_i
 - **Two** gate delays in the **AND-OR** circuit for c_{i+1}
- All **sums** can be obtained **1 gate delay after** the **carries** are **computed**.
- Independent of n , **n -bit** addition requires only **4 gate delays**.
- This is called **Carry Lookahead** adder.

Carry-lookahead adder

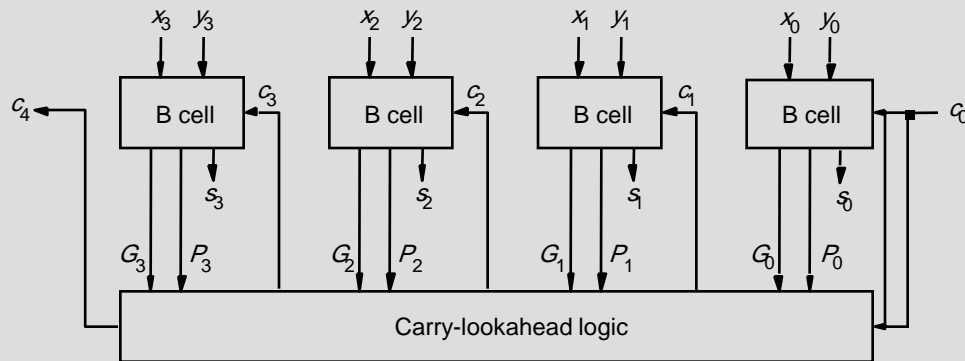

4-bit carry-lookahead adder.

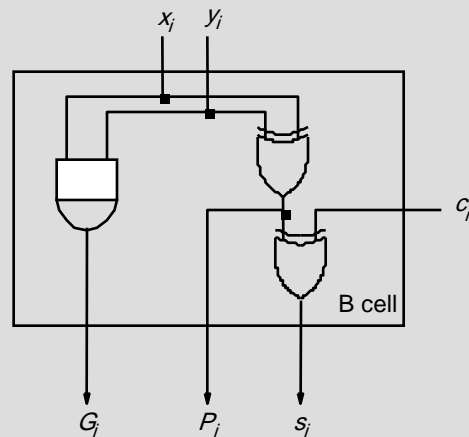

B-cell for a single stage.



Carry lookahead adder (contd..)

- Performing n -bit addition in 4 gate delays independent of n is good only **theoretically** because of **fan-in** constraints.

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- Last **AND** gate and **OR** gate require a **fan-in** of **(n+1)** for a n -bit adder.
 - ◆ For a 4-bit adder ($n=4$) **fan-in** of **5** is required.
 - ◆ **Practical limit** for most **gates**.
- In order to add operands longer than 4 bits, we can cascade 4-bit Carry-Lookahead adders. Cascade of Carry-Lookahead adders is called Blocked Carry-Lookahead adder.



Blocked Carry-Lookahead adder

Carry-out from a 4-bit block can be given as:

$$c_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

Rewrite this as:

$$P_0^I = P_3P_2P_1P_0$$

$$G_0^I = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$$


Subscript I denotes the blocked carry lookahead and identifies the block.

Cascade 4 4-bit adders, c_{16} can be expressed as:

$$c_{16} = G_3^I + P_3^I G_2^I + P_3^I P_2^I G_1^I + P_3^I P_2^I P_1^0 G_0^I + P_3^I P_2^I P_1^0 P_0^0 c_0$$



Blocked Carry-Lookahead adder (contd..)

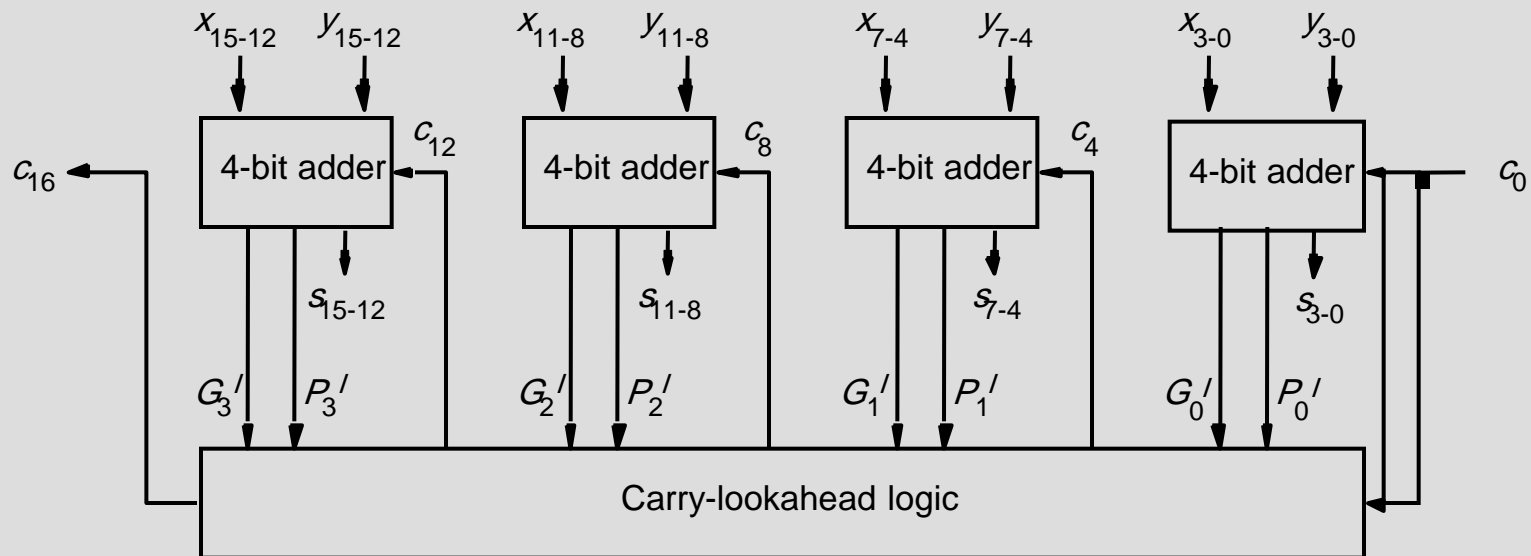

After x_i , y_i and c_0 are applied as inputs:

- G'_i and P'_i for each stage are available after 1 gate delay.
- P' is available after 2 and G' after 3 gate delays.
- All carries are available after 5 gate delays.
- c_{16} is available after 5 gate delays.
- s_{15} which depends on c_{12} is available after 8 (5+3) gate delays (Recall that for a 4-bit carry lookahead adder, the last sum bit is available 3 gate delays after all inputs are available)



Multiplication of unsigned numbers

								(13) Multiplicand M
								(11) Multiplier Q
								Partial product (PP) #1
								Partial product (PP) #2
								Partial product (PP) #3
								Partial product (PP) #4
								(143) Product P

- Product of 2 n -bit numbers is at most a $2n$ -bit number.
- We should expect to store a double-length result.

Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.




Multiplication of unsigned numbers (contd..)

- ❑ We added the partial products at end.
 - ◆ Alternative would be to add the partial products at each stage.
- ❑ Rules to implement multiplication are:
 - ◆ If the i^{th} bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
 - ◆ Hand over the partial product to the next stage
 - ◆ Value of the partial product at the start stage is 0.




Multiplication of unsigned numbers (contd..)

Typical multiplication cell

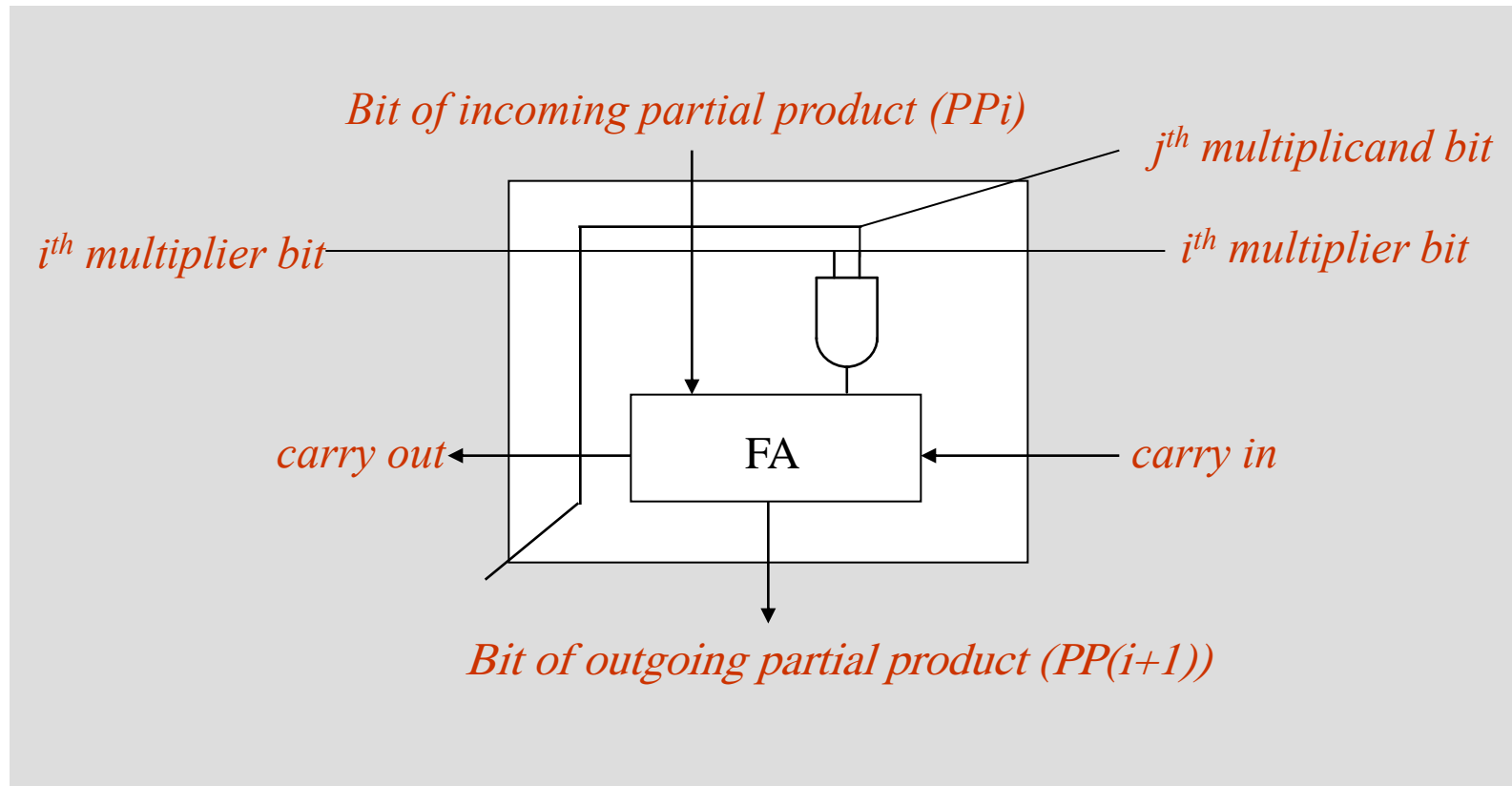

Combinatorial array multiplier

Combinatorial array multiplier

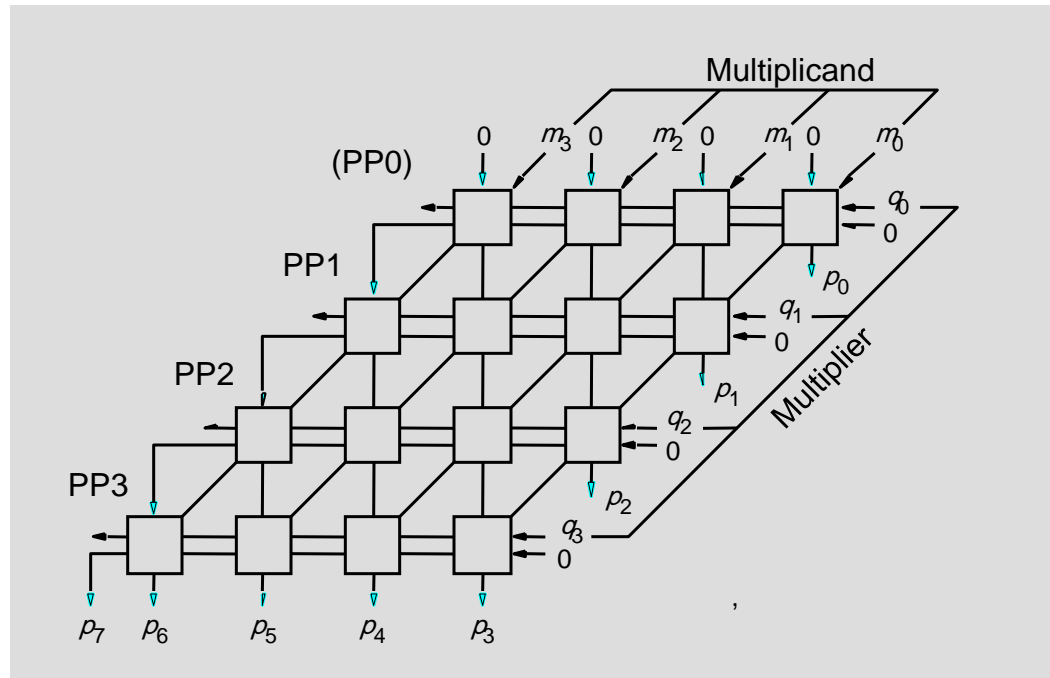

Product is: $p_7 p_6 \dots p_0$

Multiplicand is shifted by displacing it through an array of adders.



Combinatorial array multiplier (contd..)


- ❑ Combinatorial array multipliers are:
 - ◆ Extremely inefficient.
 - ◆ Have a high gate count for multiplying numbers of practical size such as 32-bit or 64-bit numbers.
 - ◆ Perform only one function, namely, unsigned integer product.
- ❑ Improve gate efficiency by using a mixture of combinatorial array techniques and sequential techniques requiring less combinational logic.



Sequential multiplication

- ❑ Recall the rule for generating partial products:
 - ◆ If the **ith** bit of the **multiplier** is **1**, **add** the appropriately **shifted multiplicand** to the **current partial product**.
 - ◆ Multiplicand has been shifted **left** when added to the partial product.
- ❑ However, adding a left-shifted multiplicand to an unshifted partial product is equivalent to **adding an unshifted multiplicand to a right-shifted partial product**.

◆ Sequential multiplication (contd..)

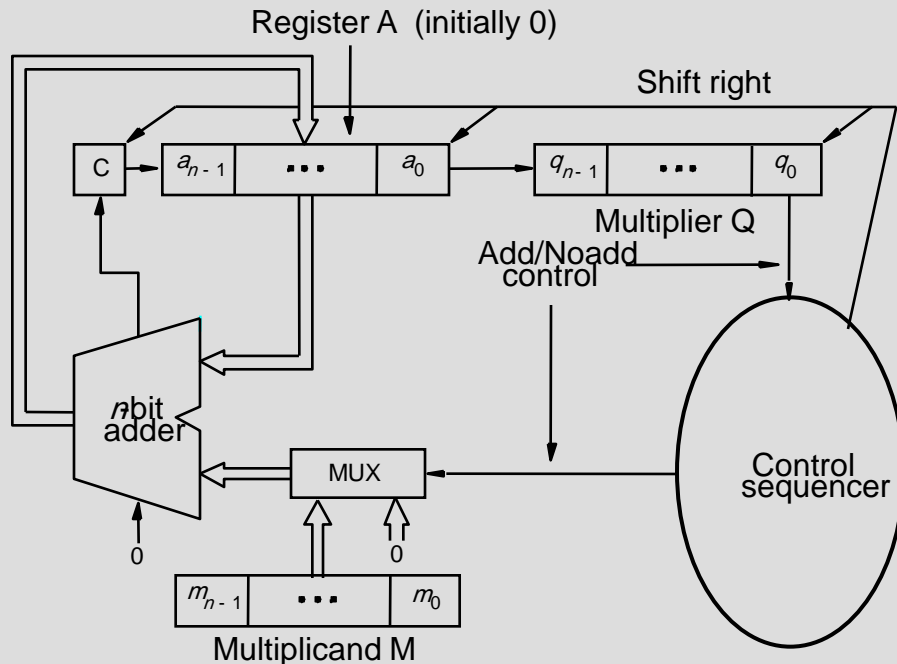

- Load Register A with 0.
- Registers are used to store multiplier and multiplicand.
- **Each cycle** repeat the following steps:

1. If the LSB $q_0=1$:
 - Add the multiplicand to A.
 - Store carry-out in flip-flop C
- Else if $q_0=0$
 - Do not add.
2. Shift the contents of register A and Q to the right, and discard q_0

Sequential multiplication (contd..)

